

Reference Sheet for C112 Hardware

Autumn 2016

1 Boolean Algebra, Gates and Circuits

Basic Operators Precedence : (strongest) $'$, \cdot , $+$ (weakest).

AND \cdot			OR $+$			NOT $'$	
A	B	R	A	B	R	A	R
0	0	0	0	0	0	0	1
0	1	0	0	1	1	1	0
1	0	0	1	0	1		
1	1	1	1	1	1		

Simplification Rules






- AND and OR are associative, commutative and distributive.
- $(A')' = A$.
- $A \cdot A' = 0$ and $A + A' = 1$.
- $A \cdot A = A$ and $A + A = A$.
- $A \cdot 0 = 0$ and $A + 1 = 1$.
- $A \cdot 1 = A$ and $A + 0 = A$.
- $(A + B)' = A' \cdot B'$ and $(A \cdot B)' = A' + B'$ (De Morgan's).

Note that:

- Each equation has a dual (swap AND with OR and 0 with 1).
- De Morgan's holds for any number of terms.


Gates

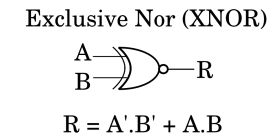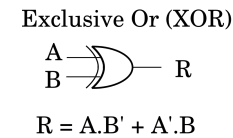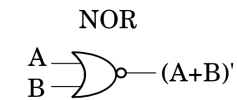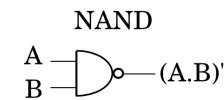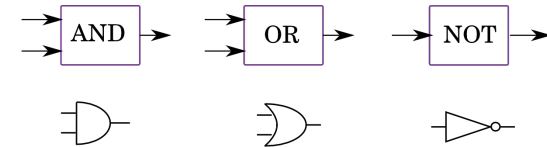There are 4 possible one-input and 16 possible two-input gates. NAND and NOR are preferred (small and fast).




Analysing Circuits Work systematically, building up a formula or truth table in stages.

Simplifying Circuits Use De Morgan's:

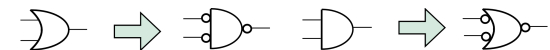

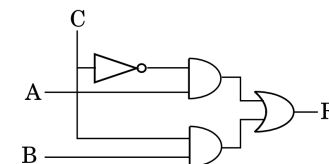Control and Data Variables E.g. in a multiplexer:



2 Combinatorial Circuits


Minterms and Maxterms

- *Minterm*: Boolean product term in which for each input, A_k , A_k or A'_k appears exactly once.
- *Maxterm*: Boolean sum term

Canonical Forms

- *Minterm Canonical Form*: Boolean sum of all minterms that output 1.
- *Maxterm Canonical Form*: Boolean product of all maxterms that output 0.

Karnaugh Maps E.g.

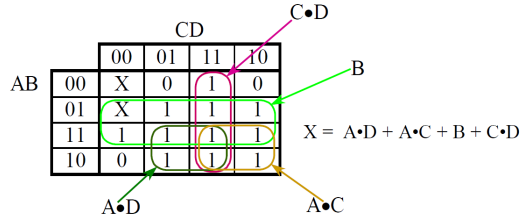

Remember:

- Order (00, 01, 11, 10) is important.
- K-maps are *cyclic*.
- We might be able to make a considerable simplification by considering *maxterms* (0s) instead of minterms.
- *Don't cares* (X) can be 0 or 1 - value depends on whether not they are circled.

Combinatorial Circuit Design Process

1. Generate the truth table.
2. Generate the Karnaugh map.
3. Find the minimal Boolean Expression:
 - (a) Read off the K-map.
 - (b) Factor out any common factors.

4. Draw the circuit.


5. Minimise to suit production method:

- (a) Reduce size (e.g. replace OR, AND by NAND, NOR).
- (b) Improve speed (reduce cycles).

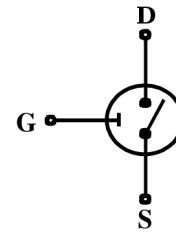6. Test the circuit (e.g. systematic testing, formal verification).

3 Physical Implementation

Models of the Transistor Need to take into account a time delay.



1. *Procedural model*:

- (a) G, D and G, S not connected.
- (b) If $V_{GS} < 0.5V$: switch open.
- (c) If $V_{GS} > 1.7V$: switch closed.


2. *Time Delay*:

- (a) It takes a constant time for the transistor to switch states - can lead to spikes.



3. *Change is not Instantaneous*:

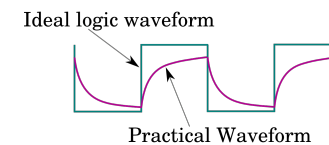- (a) Account for capacitance: $I = C \frac{dV}{dt}$.

Ideal change is 0 - 5V, but actually is somewhere close 0.2 - 3.7V (with 0.5 - 1.7V considered non-deterministic).




Basic Gate Implementations

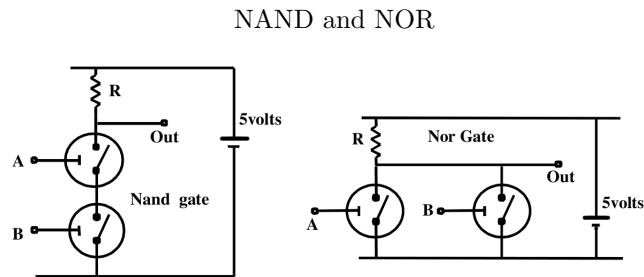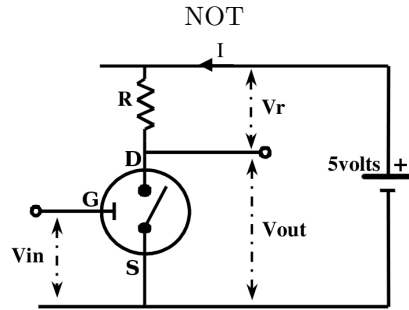


Actual ICs generally use a combination of NMOS and PMOS (Complimentary Metal Oxide Silicon) instead of resistors - lower power consumption and faster switching.

Time Dependent Behaviour of Circuits

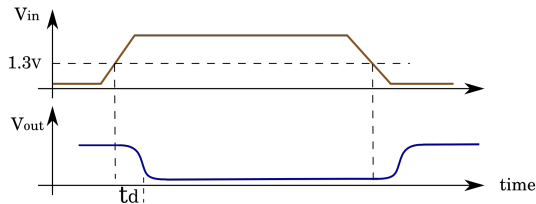

Noise Margin

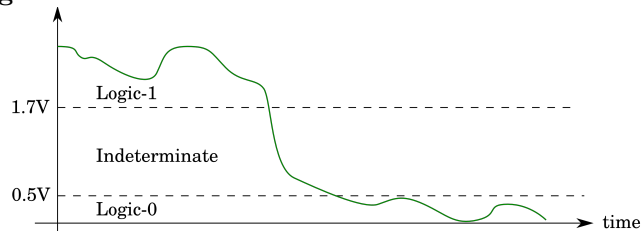


Fan out The number of inputs to which the output of a gate is connected.

- Since $\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}$ for n resistors in parallel, the load resistance decreases as fan out increases, so output voltage falls.
- Slows down circuit since capacitance is summed across all gates.


4 Synchronous Digital Systems

Feedback Circuit below could:

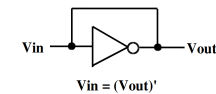


- Oscillate between values of 0 and 1.
- Settle at an intermediate value (actually $\approx 1.2V$).

The R-S Flip Flop E.g. consider:

 


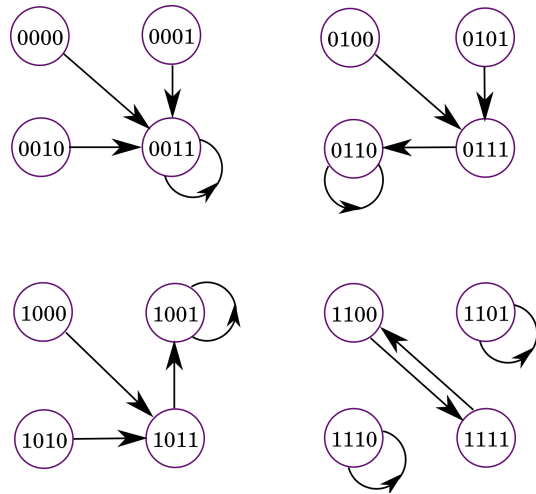By considering all possible states for (RSPQ) and what they lead to in the following time step:




- Uncertain about state at start (until set or reset).
- SR = 01: Resets memory (Q) to 0.
- SR = 10: Sets memory (Q) to 1.
- SR = 11: Keeps current state.

D-Type Latch Consider:

 


- If latch set to 1, Q becomes D .
- If latch set to 0, Q is held.

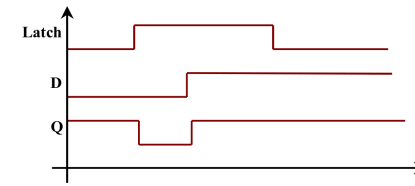
Edge Triggering D-type latch has undesirable behaviour. While latch is 1, any change on D changes Q :



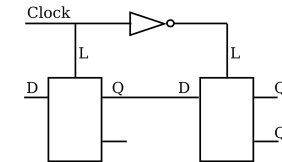Solution: edge triggered circuit: Master-Slave Flip-Flop. Now both gates cannot be open at the same time:




Flip-Flops Different types:

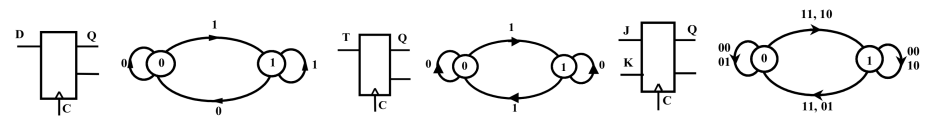

Preset and Clear

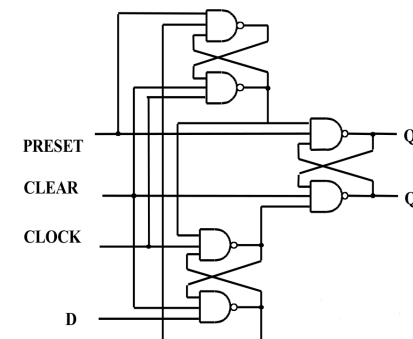
- PRESET sets Q to 1.
- CLEAR sets Q to 0.
- Behaves normally when PRESET and CLEAR both set to 1.



Synchronous Digital Systems

- *Synchronous*: Circuit only changes in response to system clock.
- *Sequential*: Goes through sequence of states.

General form:

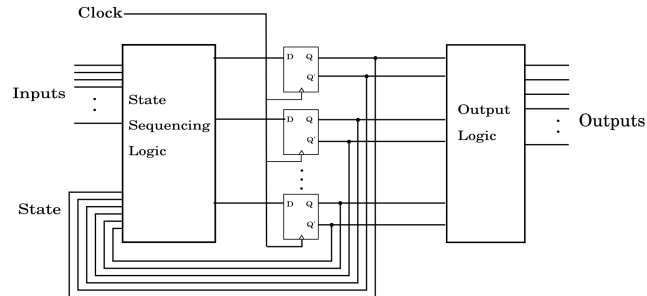

- The state sequencing logic and output logic are combinatorial circuits.
- Outputs depend only on state of circuit.
- Next state depends on current state and inputs.


Sequential Circuit Design Process

1. Determine the required number of states and assign each output to a state. Adjacent assignments should be given to states if they:
 - (a) Have the same next state for a given input.
 - (b) Are the next states of the same state.
 - (c) Or choose to minimise output logic.
2. Determine the state transitions. Draw a state transition diagram and a state transition table.
3. For each flip-flop input D_n , draw a Karnaugh Map and determine a Boolean expression in terms of the flip-flop outputs and circuit inputs. Simplify.
4. Check don't cares. Fix by one of these methods:
 - (a) Look at K-Maps and try to find a simple modification.
 - (b) Include unused states and redo.
5. Determine Boolean expressions for output from the state assignments, using Karnaugh maps.
6. Draw and optimise the circuit. Remember common terms only need to be committed to hardware once!

5 Functional Design


Shift Registers

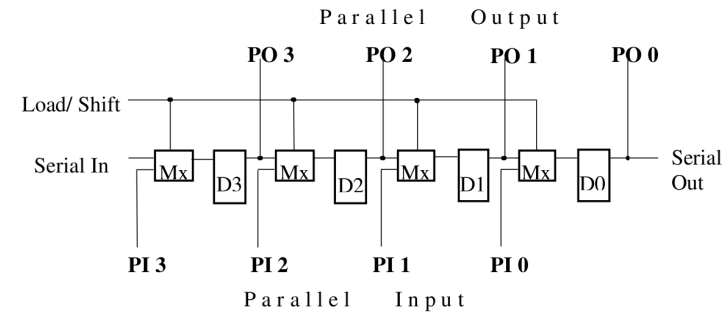- Inside a computer data is organised in a parallel form, but communication usually involves serial data.
- Registers are an ordered group of flip-flops connected to a single clock.
- We can convert parallel and serial data.




- Time to load a parallel input depends on length of register.
- Requires a separate (slower) clock to processor clock.

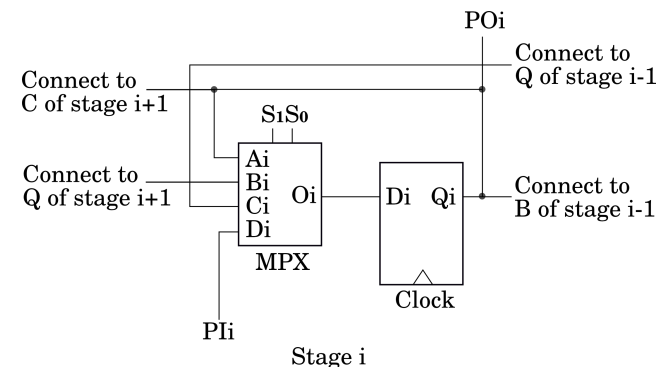Multi-Function Registers Want to be able to shift bits left / right with the same circuitry.



Here we can use 00 to hold, 01 to shift right, 10 to shift left, 11 to load parallel.

 
Dividing Clocks We can divide clocks by 2 easily:




We can stack these, one after the other, to divide by any power of 2. For non-powers of 2, we:

- Design to the next highest power of 2.
- Then use clear when the required count is reached to reset count to 0.

E.g. for 5:

 


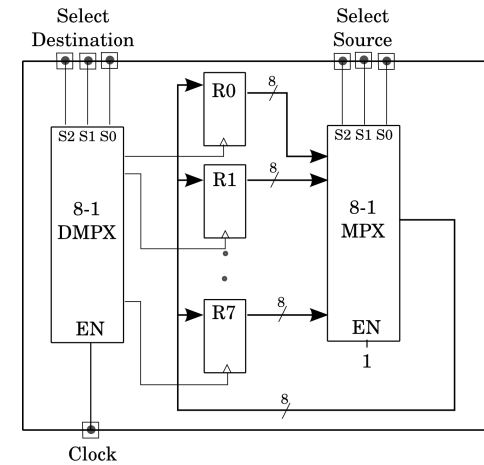Register Transfer Operations ($R_{\text{dst}} \leftarrow R_{\text{src}}$)




1. Select source register using multiplexer.
2. Select destination register using demultiplexer.
3. Transfer data from source to destination.


Multiplexers A 4-to-1 multiplexer:

 


Extended to 8-to-1 by functional design:

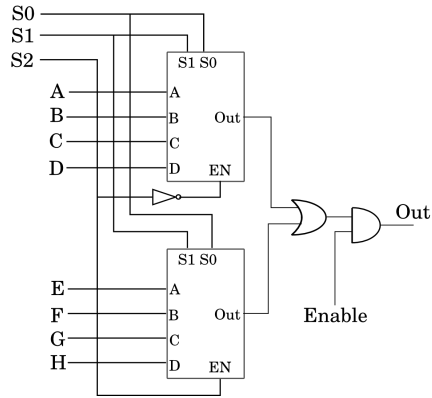


Demultiplexers A 2-to-4 demultiplexer:

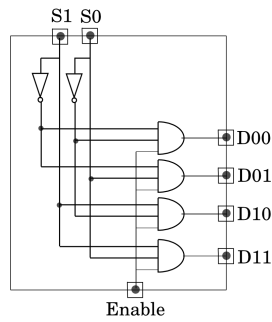


Extended to 3-to-8 by functional design:

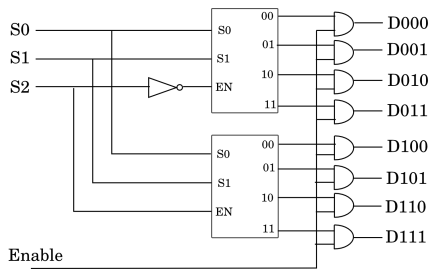

Comparators A 1-bit comparator:

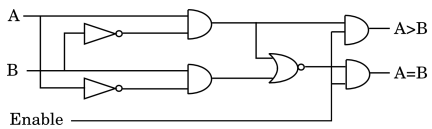


Extended to 4-bit by functional design:

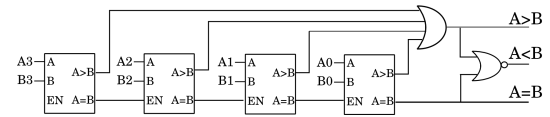

5.1 Computer Arithmetic


Half Adder $S = A \oplus B$ and $C = A \cdot B$:

A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1


 


Full Adder Need to propagate the carry, $S = A \oplus B \oplus C$ and $C_{out} = C \cdot (A \oplus B) + A \cdot B$.

A	B	C_{in}	S	C_{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1


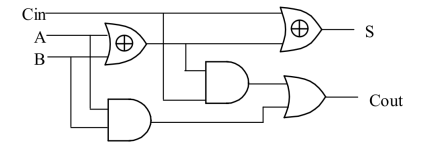


Ripple Through Carry Adder For n bits:

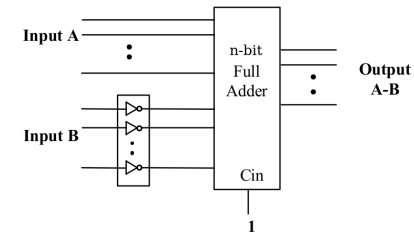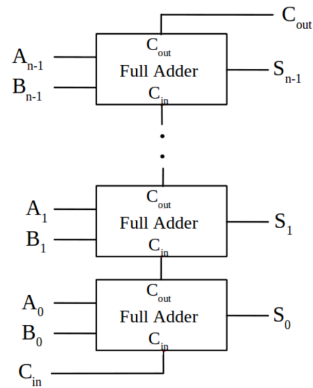

Multiplication $a_1a_0 \times b_1b_0 = a_1 \cdot b_1 \cdot 2^2 + a_0 \cdot b_1 \cdot 2 + a_1 \cdot b_0 \cdot 2 + a_0 \cdot b_0$.
Multiplication by 2 is equivalent to a left shift, so for 2 bits:

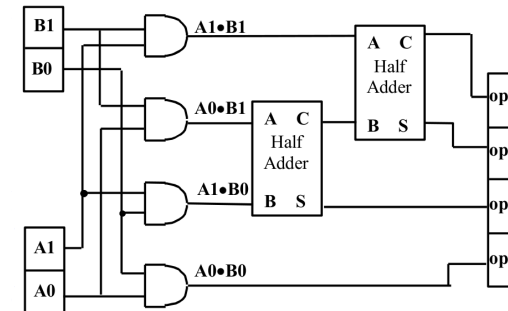
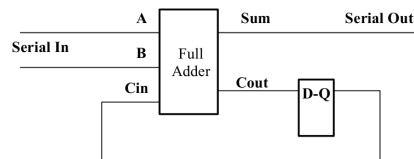
Serial Adder Assumes bits arrive least significant first.



Using functional design, for 4 bits:

Subtractor Difference = $A \oplus B \oplus P$ and Borrow = $A' \cdot (B \oplus P) + B \cdot P$:

A	B	P	Difference	Borrow
0	0	0	0	0
0	1	0	1	1
1	0	0	1	0
1	1	0	0	0
0	0	1	1	1
0	1	1	0	1
1	0	1	0	0
1	1	1	1	1

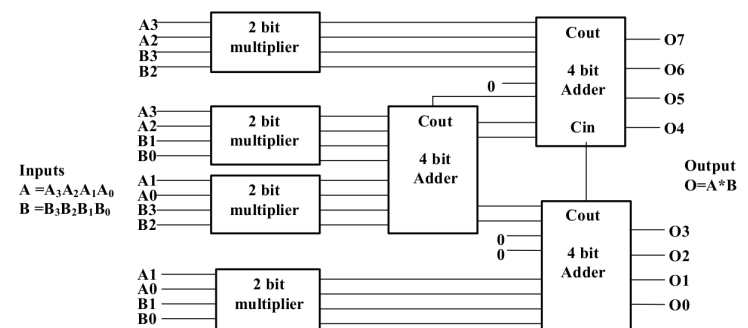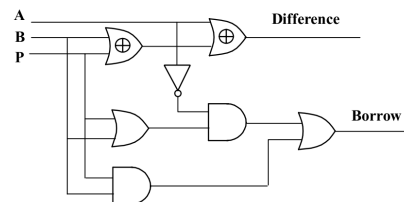


Division

- Can be done procedurally using shifts and subtracts.
- Combinatorial hardware also exists.

Subtractor using Two's Complement $A - B = A + (-B)$.

Diagram of a 4-bit ALU block. The block is labeled "ALU" and has a "Select" input at the top with three bits S2, S1, and S0. It has three 4-bit inputs: A[i], B[i], and Cin. It has two 4-bit outputs: Res[i] and Cout.

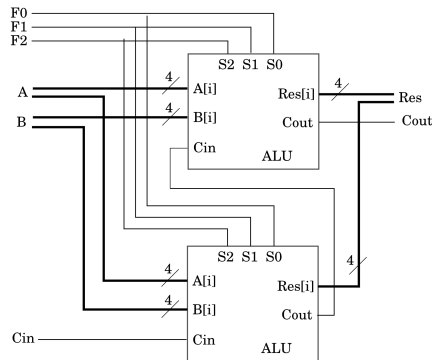We can use functional design to extend the ALU to 8 bits:



6 Processors

[illegible]

IR7	IR6	IR5	IR4	IR3	IR2	IR1	IR0
UN	F/ALU-SHIFT			UN	S/R	S/C	S/A

- 9

Execution Cycle

1. Load IR register.
2. Load A register.
3. Load B, C registers.
4. Load IR register.
5. Load RES, C registers.


Example Sequential Circuit Design For a manual processor:

1. State Assignment

Chosen to minimise output logic:

$Q_2Q_1Q_0$	State	Output
000	0	none
001	1	ClkIR
100	2	ClkA
010	3	ClkB, ClkC
101	4	ClkIR
110	5	ClkC, ClkRES


2. State Transition Diagram

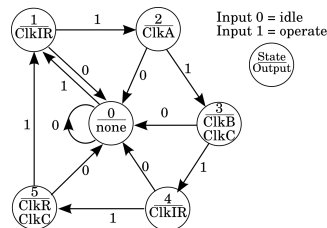

2. State Transition Table

Operate	This State	$Q_2Q_1Q_0$	Next State	D_2	D_1	D_0
0	0	000	0	0	0	0
0	1	001	0	0	0	0
0	2	100	0	0	0	0
0	3	010	0	0	0	0
0	4	101	0	0	0	0
0	5	110	0	0	0	0
0	6	011	×	×	×	×
0	7	111	×	×	×	×
1	0	000	1	0	0	1
1	1	001	2	1	0	0
1	2	100	3	0	1	0
1	3	010	4	1	0	1
1	4	101	5	1	1	0
1	5	110	1	0	0	1
1	6	011	×	×	×	×
1	7	111	×	×	×	×

 3. State Sequencing Logic - Karnaugh Maps and Boolean Eqns




4. Checking Don't Cares


Operate	This State	$Q_2Q_1Q_0$	Next State	D_2	D_1	D_0
0	6	011	0	0	0	0
0	7	111	0	0	0	0
1	6	011	4	1	0	1
1	7	111	4	1	0	1

So if the OPERATE input is at 0 when the processor is switched on, the system will begin in IDLE state.

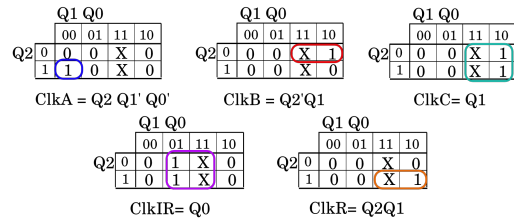5. Output Logic - Karnaugh Maps and Boolean Eqns



*. Connecting Output to the System Clock

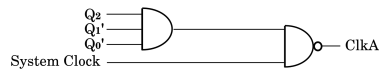


We use a NAND gate to connect each output to the system clock. This means the state register changes on the falling edge, avoiding race conditions when the next state is set on the following rising edge.

We now have a manual processor!

Memory

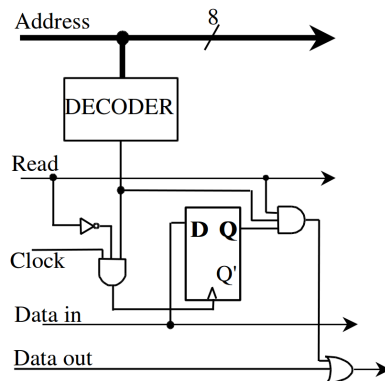
- A D-type flip flop is a one bit memory.
- We need to give it an address (binary number). We use a demultiplexer to do this.



Buses E.g. address bus, data buses, control bus.


- Data-in and data-out are never used at the same time. Convenient to use one (bi-directional) bus. This requires a tri-state buffer.

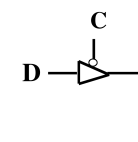Tri-State Buffer If C is 0, output follows D , otherwise is disconnected completely.



We can use a demultiplexer to make sure only one input has C set to 0.

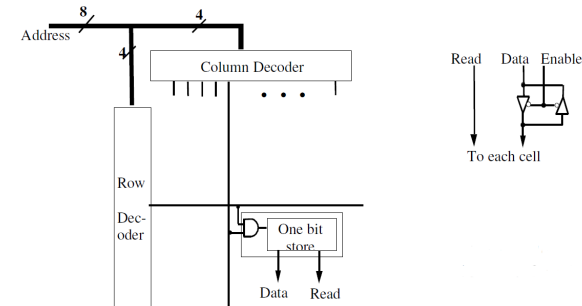
Random Access Memory Normally organised in two dimensions with row and column decoders.



- Each memory cell enabled when both row and column lines are 1.
- Only ever one such cell.
- Each cell connected to same read/write line and data line.
- Data line connected to outside through a two-way tri state buffer, so unless the chip is enabled, no data can pass in or out. Allows RAM with several chips.

Connecting RAM to a Processor

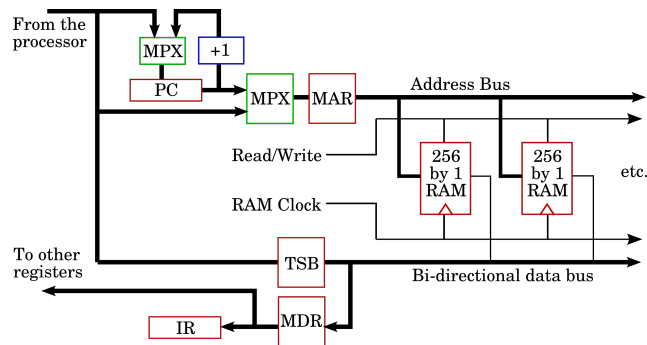- Need Memory Address Register (MAR) to store address.
- Memory Data Register (MDR) to store data read from memory / to be written to memory.
- Program counter (PC) stores address of next program instruction to be executed.
- Instruction register (IR) stores the program instruction executed.



Fetch Cycle To retrieve data from memory we go through register transfer steps. E.g. to get the next program instruction and load it into the IR:

1. $MAR \leftarrow PC$
2. $MDR \leftarrow RAM[MAR], PC \rightarrow PC + 1$
3. $IR \leftarrow MDR$

Controller

- Sets multiplexers to establish required connection paths.
- Gives falling edge signal to clock inputs of registers to be loaded (done by gating system clock - NAND with clock control logic).
- Is a synchronous sequential circuit.


Dynamic RAM For large RAMs, D-Q flip flops are too big, instead one transistor and capacitor is used for each bit. Value = whether capacitor is charged.

- Store is not permanent, ones drift to zero quickly.
- Capacitor charge is restored regularly, done by memory controller when the computer not accessing memory.

Speeding Up the Processor

- Change buses from 8 to 32 bit.
- Provide local registers which can be programmed to store partial results.
- Design a controller with as small a number of execution cycles as possible.
- Remove carry arrangements, doing arithmetic on big integers.

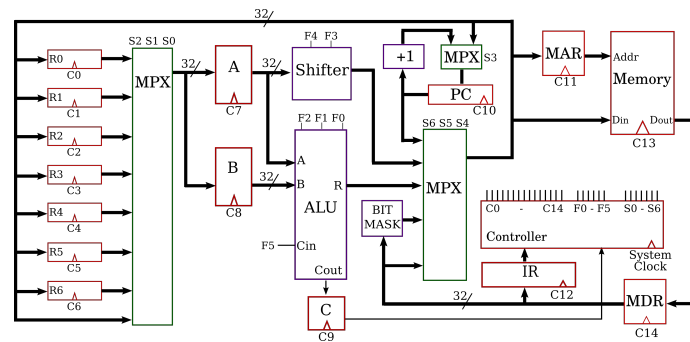- Replace bi-directional data bus with separate data in and data out buses.



Defining Operations E.g. LOAD, using register transfer language:

Instruction	Cycle	Transfers	Path
LOAD Rdst, Addr	E1	$MAR \leftarrow MDR$	Via bit mask
	E2	$MDR \leftarrow Memory$	
	E3	$Rdst \leftarrow MDR$	No mask

Instruction format: 8 bits for the opcode, 4 for Rdst, 20 for address.

Designing the Controller

- Define a control input based on how many cycles required for each operation.
 - Using 8-to-256 decoder to decode the opcode.
 - Using 3-to-8 decoder for current state.
- Sequential design problem to work out next state, uses this control input and previous state.
- Output logic:
 - Clocks: NAND gates with system clock. In practice, we can simplify output logic by considering the following cycle.
 - Multiplexers and ALU / Shifter function selection output is trivial.

Possible Improvements

- Instructions packed on byte boundaries so not to waste fetch cycles.
- Additional arithmetic hardware.
- Additional multiplexers, e.g. to select input of B independently of A.